

FDTD Simulation of Lossless Transmission Lines



UNIVERSITEIT
GENT

Bram Popelier, Constantijn Coppers, Vincent Belpaire
Supervisors: Prof. Dries Vande Ginste, ir. Emile Vanderstraeten
Dec. 23, 2022

University of Ghent
Faculty of Engineering and Architecture
Bachelor of Science: Biomedical Engineering

Abstract

Short review of the report.

1 The update functions

The update functions are given as:

$$\tilde{I}_{n+\frac{1}{2}}^{m+\frac{1}{2}} = \tilde{I}_{n+\frac{1}{2}}^{m-\frac{1}{2}} + \alpha (V_n^m - V_{n+1}^m), \quad V_n^{m+1} = V_n^m + \alpha \left(\tilde{I}_{n-\frac{1}{2}}^{m+\frac{1}{2}} - \tilde{I}_{n+\frac{1}{2}}^{m+\frac{1}{2}} \right), \quad (1)$$

where

$$\alpha \triangleq \frac{v\Delta t}{\Delta z} \quad (2)$$

is the dimensionless Courant factor and

$$\tilde{I}_{n+\frac{1}{2}}^{m+\frac{1}{2}} = I_{n+\frac{1}{2}}^{m+\frac{1}{2}} R_c \quad (3)$$

is the rescaled current.

At the boundaries the update function for V takes another form.

- At $z = 0$

The voltage update function is given as:

$$V_0^{m+1} = V_0^m + \frac{2\Delta t}{C\Delta z} \left(I_g^{m+\frac{1}{2}} - I_{\frac{1}{2}}^{m+\frac{1}{2}} \right), \quad (4)$$

with

$$I_g^{m+\frac{1}{2}} = \frac{E_g^{m+\frac{1}{2}}}{R_g} - \frac{V_0^m + V_0^{m+1}}{2R_g}. \quad (5)$$

Substituting (4) in (3) and using (1), the two relations $v = \frac{1}{\sqrt{LC}}$ and $R_c = \sqrt{\frac{L}{C}}$ and the new defined constant $\tilde{R}_g = \frac{R_c}{R_g}$ yields, after some rearrangements:

$$V_0^{m+1} = C_1 V_0^m + C_2 \left(E_g^{m+\frac{1}{2}} \tilde{R}_g - \tilde{I}_{\frac{1}{2}}^{m+\frac{1}{2}} \right) \quad (6)$$


where

$$C_1 = \frac{1 - \alpha \tilde{R}_g}{1 + \alpha \tilde{R}_g}, \quad (7)$$

$$C_2 = \frac{2\alpha}{1 + \alpha \tilde{R}_g}, \quad (8)$$

are two dimensionless constants.

- At $z = l$

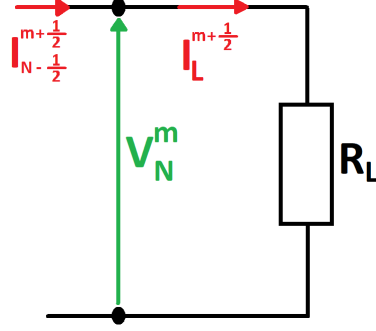

The voltage update function becomes:

$$V_N^{m+1} = V_N^m + \frac{2\Delta t}{C\Delta z} \left(I_{N-\frac{1}{2}}^{m+\frac{1}{2}} - I_L^{m+\frac{1}{2}} \right) \quad (9)$$

Kirchoff's voltage law in discretized form states that

$$I_L^{m+\frac{1}{2}} = \frac{V_N^{m+\frac{1}{2}}}{R_L} \quad (10)$$

$$= \frac{V_N^m + V_N^{m+1}}{2R_L} \quad (11)$$

Substituting (10) in (8) and using the same relations as for $z = 0$ and the new defined constant $\tilde{R}_L = \frac{R_c}{R_L}$ yields, after some rearrangements:

$$V_N^{m+1} = C_3 V_N^m + C_4 I_{N-\frac{1}{2}}^{m+\frac{1}{2}}, \quad (12)$$


where

$$C_3 = \frac{1 - \alpha \tilde{R}_L}{1 + \alpha \tilde{R}_L}, \quad (13)$$

$$C_4 = \frac{2\alpha}{1 + \alpha \tilde{R}_L}, \quad (14)$$

are two dimensionless constants.

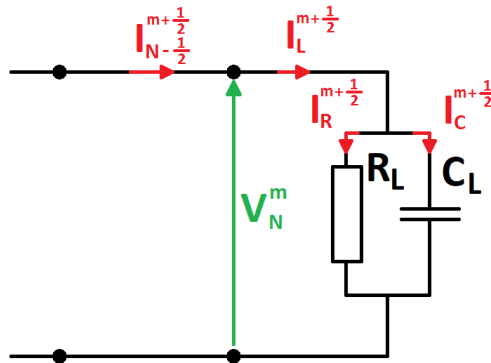Now if there would be a capacitor added to the load the following situation will occur



Kirchoff's current law states that

$$I_L^{m+\frac{1}{2}} = I_R^{m+\frac{1}{2}} + I_C^{m+\frac{1}{2}}. \quad (15)$$

Using Kirchoff's voltage law at the resistor gives

$$I_R^{m+\frac{1}{2}} = \frac{V_N^{m+\frac{1}{2}}}{R_L} \quad (16)$$

$$= \frac{V_N^m + V_N^{m+1}}{2R_L} \quad (17)$$

The relation between the current and the voltage at the capitor is given as

$$\hat{i} = -C \frac{\partial \hat{v}}{\partial t}. \quad (18)$$

For a first order FDM this turns into

$$I_R^{m+\frac{1}{2}} = -C_L \frac{V_N^{m+1} - V_N^m}{\Delta t}. \quad (19)$$

Substituting (16) and (18) into (14) gives

$$I_L^{m+\frac{1}{2}} = \left(\frac{1}{2R_L} - \frac{C_L}{\Delta t} \right) V_N^{m+1} + \left(\frac{1}{2R_L} + \frac{C_L}{\Delta t} \right) V_N^m \quad (20)$$

and can be rewritten as

$$\tilde{I}_L^{m+\frac{1}{2}} = \frac{\tilde{Z}_1}{2} V_N^{m+1} + \frac{\tilde{Z}_2}{2} V_N^m \quad (21)$$

with

$$\tilde{Z}_1 = R_C \left(\frac{1}{R_L} - 2 \frac{C_L}{\Delta t} \right) \quad (22)$$

$$\tilde{Z}_2 = R_C \left(\frac{1}{R_L} + 2 \frac{C_L}{\Delta t} \right) \quad (23)$$

Substituting (20) into the adjusted voltage update function at $z = l$ yields

$$V_N^{m+1} = C'_3 V_N^m + C'_4 \tilde{I}_{N-\frac{1}{2}}^{m+\frac{1}{2}}, \quad (24)$$

where

$$C'_3 = \frac{1 - \alpha \tilde{Z}_2}{1 + \alpha \tilde{Z}_1}, \quad (25)$$

$$C'_4 = \frac{2\alpha}{1 + \alpha \tilde{Z}_1}. \quad (26)$$

Notice when $C_L = 0$ then $C'_3 = C_3$ and $C'_4 = C_4$.